

# Dayananda Sagar College of Engineering

## Department of Electronics and Communication Engineering Shavige Malleshwara Hills, Kumaraswamy Layout, Bengaluru – 560 078.

(An Autonomous Institute affiliated to VTU, Approved by AICTE & ISO 9001:2008 Certified)

Accredited by National Assessment and Accreditation Council (NAAC) with 'A' grade

#### **OPEN ENDED EXPERIMENT**

Course: ABNC-IV Laboratory (DIGITAL CIRCUIT DESIGN WITH FPGA- HDL LAB)

Semester: 4
Date:

Course Code: 22ECL471

Lab Batch: A3

A Report on

**DECADE COUNTERS** 

Submitted by

1DS22EC052 1DS22EC054 BHUVAN KUMAR S CHAITRA KRISHNA GOUDA

Faculty In-charge Prof. Manasa R. K. Prof. Ninu Rachel Philip

**Signature of Faculty In-charge** 

#### DEVELOP A VERILOG CODE FOR THE DECADE COUNTER

#### **INTRODUCTION:**

In the field of digital electronics, counters are integral components widely used in various applications such as digital clocks, frequency counters, and event counters. Among these, the decade counter holds a significant place due to its ability to count from 0 to 9 cyclically. This report delves into the design and implementation of a decade counter using Verilog, a hardware description language (HDL) known for its effectiveness in digital system design.


A decade counter, also known as a mod-10 counter, it is a digital circuit that counts the number of pulses or clock signals it receives, incrementing its output by one for every ten input pulses. The design of a decade counter typically involves flip-flops, which are basic memory elements in digital electronics. By connecting flip-flops in a specific configuration, we can create a counter that progresses through a defined sequence of states. It is a type of asynchronous counter, which means that the output of each stage is used as the input for the next stage, allowing the counter to count in a sequential manner. It is a type of counter that counts ten distinct states, typically from 0 to 9. Once it reaches its maximum count, it resets to zero and starts the counting a new cycle. This functionality makes it ideal for applications requiring precise timing and sequence control.

Decade counters are commonly used in digital systems and electronic devices, such as digital clocks, timers, and frequency dividers, to count events or measure time intervals. They are typically designed to count up to a maximum value of nine, after which they reset to zero, ready to start counting again.

Verilog, as an HDL, provides a robust platform for describing digital systems and is widely used for designing and verifying digital circuits. The language allows designers to describe the behavior and structure of electronic systems at multiple levels of abstraction, from the algorithmic level down to the gate level. Verilog's capability to simulate the behavior of a digital circuit before actual hardware implementation ensures that designs are error-free and optimized for performance.

By the end of this report, readers will have a comprehensive understanding of how to design and implement a decade counter using Verilog.

## **DESIGN:**

 

# TRUTH TABLE:

Clock Count	Output bit Pattern				Decimal Value
	QD	Qc	Q <sub>B</sub>	QA	
1	0	0	0	0	0
2	0	0	0	1	1
3	0	0	1	0	2
4	0	0	1	1	3
5	0	1	0	0	4
6	0	1	0	1	5
7	0	1	1	0	6
8	0	1	1	1	7
9	1	0	0	0	8
10	1	0	0	1	9
11	Counter Resets its Output back to zero				

# **PROGRAM:**

VERILOG CODE	TESTBENCH		
module decade_counter(en, clock, count);	`timescale 1ns/1ps		
input en, clock;	module decadecounter_tb;		
output reg [3:0] count;	wire [3:0] count;		
always @( posedge clock)	reg en,clock;		
begin	decade_counter dut(.en(en), .clock(clock),		
if(en)	.count(count));		
begin	initial begin		
if ( count>=4'd0 && count<4'd10)	\$display(\$time, " << Starting the Simulation >>");		
count<=count+4'd1;	en=0;		
else	clock=0;		
count<=4'd0;	#20 en=1'd1;		
end	end		
else	always		
count<=4'd0;	#5 clock=~clock;		
end	initial		
endmodule	\$monitor ( \$time , "clock= %b, count= %d, en=		
	%b", clock,count, en);		
	endmodule		

### **RTL CODE:**

```
module decoder_counter(clk, rst, q);
input clk, rst;
output [3:0]q;
reg [3:0]q;
reg clkdiv;
reg[22:0] div;
initial q = 4'd0;
always @ (posedge clk)
begin
div=div+1'd1;
clkdiv=div[22];
end
always@(posedge clkdiv or posedge rst)
begin
if (rst == 1'd1)
q = 4'd0;
else if (q== 4'd9)
q = 4'd0;
else
q=q+1;
end
endmodule
(Advance ) Verilog Code of Decade Counter:
module decade_counter ( output reg [3:0] q,
input clk);
always @(posedge clk)
q \le q = 9?0:q+1;
endmodule
```

### **PIN ASSIGNMENT:**

clock: set\_location\_assignment PIN\_P11 -to CLOCK\_50

rst: set\_location\_assignment PIN\_C10 -to SW[0]


q[3]: set\_location\_assignment PIN\_A8 -to LEDR[0]

**q[2]:** set\_location\_assignment PIN\_A9 -to LEDR[1]

**q[1]:** set\_location\_assignment PIN\_A10 -to LEDR[2]

**q[0]:** set\_location\_assignment PIN\_B10 -to LEDR[3]

#### **RTL Viewer:**

 

## **SIMULATION RESULTS:**



### **APPLICATIONS:**

- 1. Digital Clocks: Decade counters are used to display hours, minutes, and seconds in digital clocks.
- **2. Timers:** Decade counters are used to implement timers that count down from a set value to zero.
- **3. Frequency Division:** Decade counters can be used to divide a high-frequency signal by 10, generating a lower-frequency signal.
- **4. Medical Devices:** Decade counters are used in medical devices, such as heart rate monitors and blood pressure monitors.
- **5. Aerospace:** Decade counters are used in aerospace applications, such as counting navigation data and sensor readings.

#### **RESULT DISCUSSION:**

Design and Simulated Decade Counter with Verilog Code using FPGA implementation.

### **CONCLUSION:**

In conclusion, the decade counter project exemplifies the effective use of Verilog and FPGA technology in digital design. The design and implementation of a decade counter using Verilog and FPGA highlight the synergy between hardware description languages and reprogrammable hardware platforms.